

Lewis Collum - Clarkson University

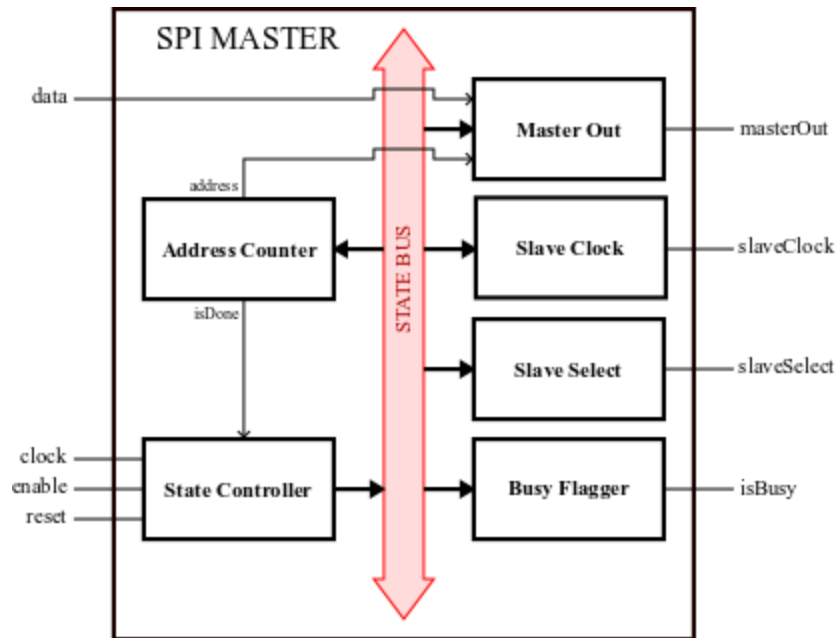


Figure 1. Conceptual model for the SPI master controller. This controller takes in a clock and the data to send, and outputs the slave clock, slave select and the master out, as well as a “busy” flag.

 


Figure 2. Illustrates *master out* correctly fetching data.

A. *common.vhdl*

This package creates types that are used throughout the project.

1. ***stateType*** is an enumeration for the states.
2. ***word*** is the length of the data to be sent.
3. ***counter*** is used in the *Address Counter* (figure 1) to create an unsigned with a max value that is the length of ***word***.
4. ***validFrequencyRange*** is the valid frequency range for the Sparkfun Seven-Segment Display.

```
library ieee;
use ieee.numeric_std.all;
use ieee.math_real.log;

package common is
    type stateType is (idle, selecting, fetching, receiving, stopping, disabled);
    subtype word is unsigned(15 downto 0);
    subtype counter is unsigned(integer(log((real(word'length)) / log(real(2)))-0.5) downto 0);
    subtype validFrequencyRange is integer range 1 to 500e3;
end package common;
```

B. SPIMaster.vhdl

Contains modules: *Busy Flagger*, *State Controller*, *Slave Clock*, *Slave Select*, and *Master Out* (figure 1). Each of these modules is a process. These processes should be extracted into their own VHDL entity to improve encapsulation and readability.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

library work;
use work.common.all;

entity SPIMaster is
    generic(
        constant slaveClockPolarity: std_logic);
    port(
        clock: in std_logic;
        data: in word;
        resetActiveLow: in std_logic;
        enable: in std_logic;
        isBusy: out std_logic;
        masterOut: out std_logic;
        slaveClock: buffer std_logic;
        slaveSelectActiveLow: out std_logic);
end SPIMaster;

architecture CPHA0 of SPIMaster is
    component SPIAddressCounter is
        port(
            state: inout stateType;
            address: buffer counter;
            isDone: out std_logic);
    end component SPIAddressCounter;

    signal dataBitAddress: counter;
    signal state: stateType;
    signal isCounterDone: std_logic;

begin
    stateControl : process(clock, isCounterDone)
        procedure handleCounterInterrupt;
        procedure updateAllStates;
        procedure updateCyclicalStates;
        impure function isReadyToSelect return boolean;
        impure function isReadyToFetch return boolean;
        impure function isReadyToReceive return boolean;
        impure function isReadyToIdle return boolean;
        impure function isLastBitOfData return boolean;

        procedure handleCounterInterrupt is begin
            state <= stopping;
        end procedure handleCounterInterrupt;

        procedure updateAllStates is begin
            if resetActiveLow = '0' then
                state <= idle;
            elsif enable = '1' then
                updateCyclicalStates;
            else
                state <= disabled;
            end if;
        end procedure updateAllStates;
```

```

    procedure updateCyclicalStates is begin
        if isReadyToIdle then
            state <= idle;
        elsif isReadyToSelect then
            state <= selecting;
        elsif isReadyToFetch then
            state <= fetching;
        elsif isReadyToReceive then
            state <= receiving;
        end if;
    end procedure updateCyclicalStates;

    impure function isReadyToSelect return boolean is begin
        return state = idle;
    end function isReadyToSelect;

    impure function isReadyToFetch return boolean is begin
        return state = receiving;
    end function isReadyToFetch;

    impure function isReadyToReceive return boolean is begin
        return state = fetching or state = selecting;
    end function isReadyToReceive;

    impure function isReadyToIdle return boolean is begin
        return state = stopping;
    end function isReadyToIdle;

    impure function isLastBitOfData return boolean is begin
        return dataBitAddress = dataBitAddress'low;
    end function isLastBitOfData;
begin
    if rising_edge(isCounterDone) then
        handleCounterInterrupt;
    elsif rising_edge(clock) then
        updateAllStates;
    end if;
end process stateControl;

slaveClock_StateMachine : process(state)
    procedure reset is begin
        slaveClock <= slaveClockPolarity;
    end procedure reset;

    procedure trailingEdge is begin
        slaveClock <= slaveClockPolarity;
    end procedure trailingEdge;

    procedure leadingEdge is begin
        slaveClock <= not slaveClockPolarity;
    end procedure leadingEdge;
begin
    case state is
        when idle | stopping =>
            reset;
        when fetching =>
            trailingEdge;
        when receiving =>
            leadingEdge;
        when others =>
            null;
    end case;
end process slaveClock_StateMachine;

```

```

slaveSelect_StateMachine : process(state)
    procedure deselectSlave is begin
        slaveSelectActiveLow <= '1';
    end procedure deselectSlave;

    procedure selectSlave is begin
        slaveSelectActiveLow <= '0';
    end procedure selectSlave;
begin
    case state is
        when idle =>
            deselectSlave;
        when selecting =>
            selectSlave;
        when others =>
            null;
    end case;
end process slaveSelect_StateMachine;

masterOut_StateMachine : process(state)
    procedure fetchBit is begin
        masterOut <= data(to_integer(dataBitAddress));
    end procedure fetchBit;

    procedure releaseBit is begin
        masterOut <= '-';
    end procedure releaseBit;
begin
    case state is
        when idle | stopping =>
            releaseBit;
        when fetching | selecting =>
            fetchBit;
        when others =>
            null;
    end case;
end process masterOut_StateMachine;

isBusy_StateMachine: process(state)
begin
    case state is
        when idle =>
            isBusy <= '0';
        when selecting =>
            isBusy <= '1';
        when others =>
            null;
    end case;
end process isBusy_StateMachine;

dataBitAddressCounter: SPIAddressCounter
    port map(
        state => state,
        address => dataBitAddress,
        isDone => isCounterDone);

end CPHA0;

```

C. SPIAddressCounter.vhdl

Generates the address of the bit that is being read from the data. Also sends an interrupt when done.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

library work;
use work.common.all;

entity SPIAddressCounter is
    port(
        state: in stateType;
        address: buffer counter;
        isDone: out std_logic);
end SPIAddressCounter;

architecture countDown of SPIAddressCounter is
    signal isLastFetch: std_logic;
    signal isLastReceive: std_logic;
begin
    stateControl: process(state)
        procedure resetCounter is begin
            address <= to_unsigned(word'high, address'length);
        end procedure resetCounter;

        procedure resetFlags is begin
            isLastFetch <= '0';
            isLastReceive <= '0';
        end procedure resetFlags;

        procedure decrementCounter is begin
            address <= address - 1;
        end procedure decrementCounter;

        procedure updateOnFetch is begin
            if address = 0 then
                isLastFetch <= '1';
            end if;
        end procedure updateOnFetch;

        procedure updateOnReceive is begin
            if isLastFetch = '1' then
                isLastReceive <= '1';
            else
                decrementCounter;
            end if;
        end procedure updateOnReceive;

    begin
        case state is
            when idle =>
                resetCounter;
                resetFlags;
            when fetching =>
                updateOnFetch;
            when receiving =>
                updateOnReceive;
            when others =>
                null;
        end case;
    end process stateControl;

    setIsDoneInterrupt: process(state)
    begin
```

```
        if isLastReceive = '1' then
            isDone <= '1';
        else
            isDone <= '0';
        end if;
    end process setIsDoneInterrupt;
end architecture countDown;
```

D. timingUtil.vhdl

Helper package for testing.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

package TimingUtil is
    function frequencyToPeriod(frequency: integer) return time;
    procedure generateClock(signal clock: out std_logic; frequency: integer);
    procedure highPulseForTime(signal output: out std_logic; duration: time);
    procedure lowPulseForTime(signal output: out std_logic; duration: time);
end package TimingUtil;

package body TimingUtil is

    function frequencyToPeriod(frequency: integer) return time is
    begin
        return 1 sec / frequency;
    end function frequencyToPeriod;

    procedure generateClock(signal clock: out std_logic; frequency: integer) is
        constant period: time := 1 sec / frequency;
        constant halfPeriod: time := period / 2;
    begin
        loop
            clock <= '1';
            wait for halfPeriod;
            clock <= '0';
            wait for halfPeriod;
        end loop;
    end procedure generateClock;

    procedure highPulseForTime(signal output: out std_logic; duration: time) is
    begin
        output <= '1';
        wait for duration;
        output <= '0';
    end procedure highPulseForTime;

    procedure lowPulseForTime(signal output: out std_logic; duration: time) is
    begin
        output <= '0';
        wait for duration;
        output <= '1';
    end procedure lowPulseForTime;

end package body TimingUtil;
```


E. Test_SPIMaster.vhdl

Test Entity for SPIMaster

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

library work;
use work.common.all;
use work.timingUtil.all;

entity Test_SPIMaster is
end entity Test_SPIMaster;

architecture simulation of Test_SPIMaster is
  component SPIMaster is
    generic(
      constant slaveClockPolarity: std_logic);
    port(
      clock: in std_logic;
      data: in word;
      resetActiveLow: in std_logic;
      enable: in std_logic;
      isBusy: out std_logic;
      masterOut: out std_logic;
      slaveClock: buffer std_logic;
      slaveSelectActiveLow: out std_logic);
  end component SPIMaster;

  constant clockFrequency: validFrequencyRange := 250e3;
  constant clockPeriod: time := frequencyToPeriod(clockFrequency);

  signal clock: std_logic;
  signal dataToSend: word;
  signal resetActiveLow: std_logic;
  signal enable: std_logic;
  signal isBusy: std_logic;
  signal masterOut, slaveClock, slaveSelectActiveLow: std_logic;

begin

  generateClock(clock, frequency => clockFrequency);

  uut: SPIMaster
    generic map(
      slaveClockPolarity => '0')
    port map(
      clock => clock,
      data => dataToSend,
      resetActiveLow => resetActiveLow,
      enable => enable,
      isBusy => isBusy,
      masterOut => masterOut,
      slaveClock => slaveClock,
      slaveSelectActiveLow => slaveSelectActiveLow);

  test : process is
    constant testWord: word := x"A4E1";

    procedure setup is
    begin
      enable <= '1';
      lowPulseForTime(resetActiveLow, clockPeriod/2);
    end procedure setup;
```

```

procedure testFetchWord is
begin
    setup;
    dataToSend <= testWord;
    wait for clockPeriod*2*19;
end procedure testFetchWord;

procedure testResetWhileFetching is
begin
    setup;
    dataToSend <= testWord;
    wait for 6*clockPeriod;
    lowPulseForTime(resetActiveLow, clockPeriod);
    wait for clockPeriod*10;
end procedure testResetWhileFetching;

procedure testDisableWhileFetching is
begin
    setup;
    dataToSend <= testWord;
    wait for 6*clockPeriod;
    lowPulseForTime(enable, 4*clockPeriod);
    wait for 8*clockPeriod;
end procedure testDisableWhileFetching;

begin
    testFetchWord;`
    report "END OF TEST" severity failure; --TODO figure out best practice to end a test properly.
end process test;

end architecture simulation;

```